

---

# Feedback and Flip-Flops

Philipp Koehn

7 September 2019



# The Story So Far

1



- We can encode numbers

# The Story So Far

1



- We can encode numbers
- We can do calculation

# The Story So Far

1



- We can encode numbers
- We can do calculation
- ... but it's all a bit static

# The Story So Far



1

- We can encode numbers
- We can do calculation
- ... but it's all a bit static
- How about a counter?


# The Story So Far



- We can encode numbers
- We can do calculation
- ... but it's all a bit static
- How about a counter?
  - this requires "memory"


# feedback

# A Strange Contraption

 




# Let's Turn It On

 

Electricity is on  $\rightarrow$  this opens the normally closed key

# Let's Turn It On

 

Electricity is off → this closes the normally closed key

# What Do We Have?

6



- A Buzzer


# What Do We Have?

6



- A Buzzer


- A Clock

 


# What Do We Have?

- A Buzzer

- A Clock

 

- An Oscillator

 

(symbol)

# Oscillator




- **Period** of oscillator
- Frequency: cycles per second
- Unit: 1 cycle per second: 1 Hertz
- Modern computes:  
Billions of Hertz = Gigahertz (GHz)



Heinrich Hertz  
1857--1894

flip flop


# Another Contraption

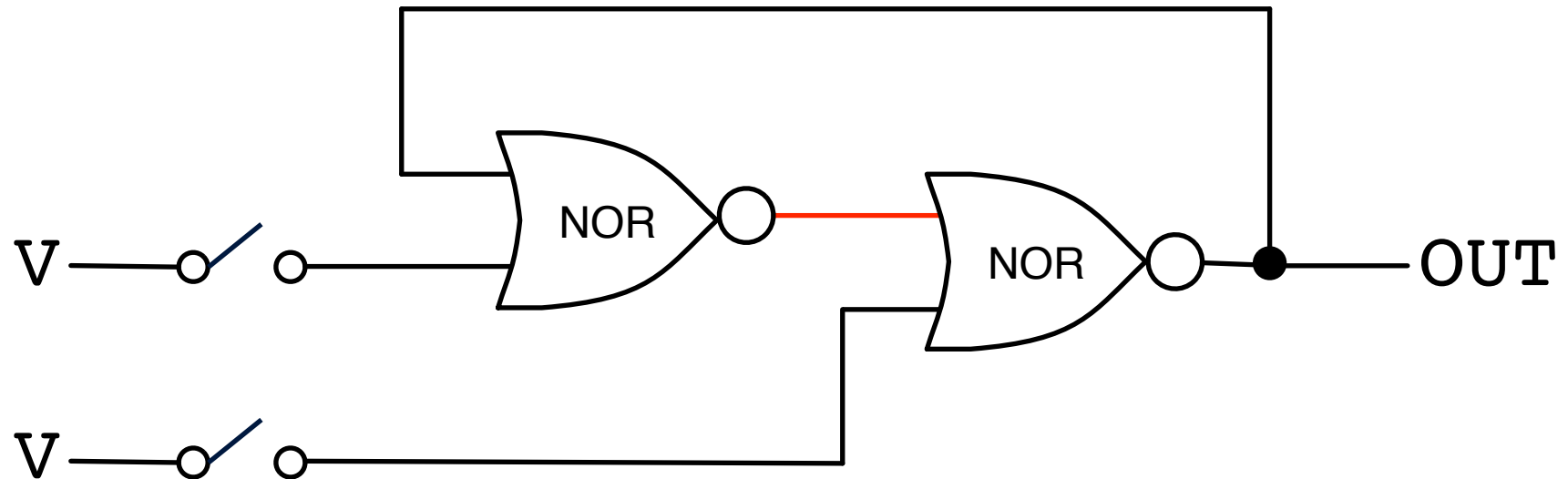




# Closing Upper Key

10

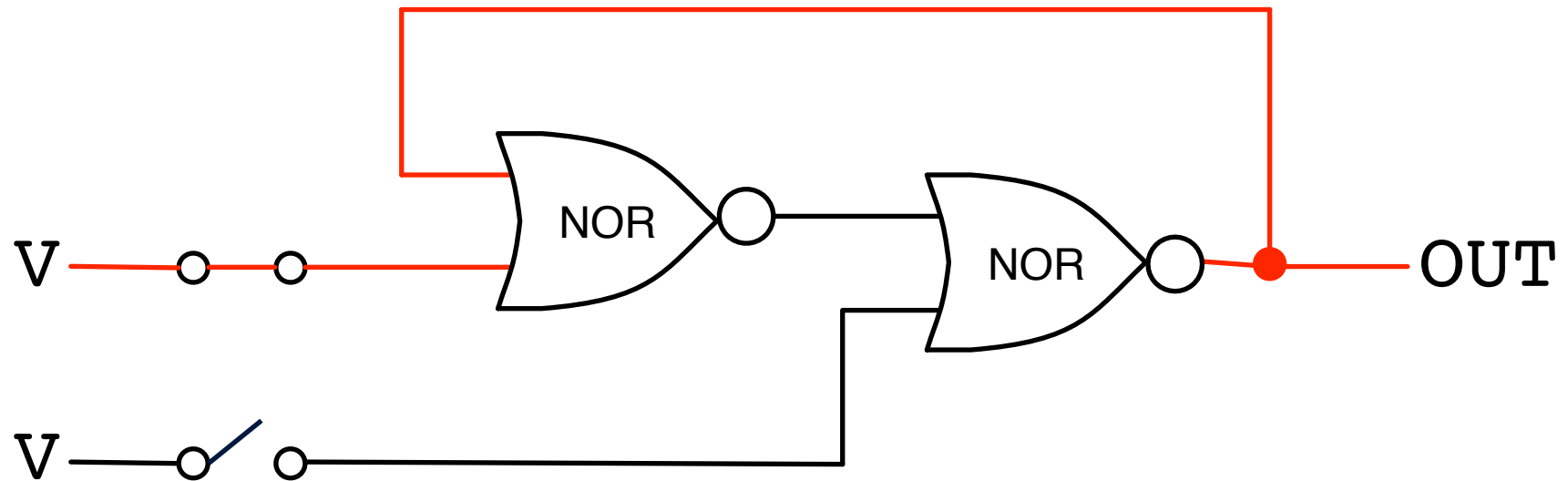

# Opening Upper Key

11

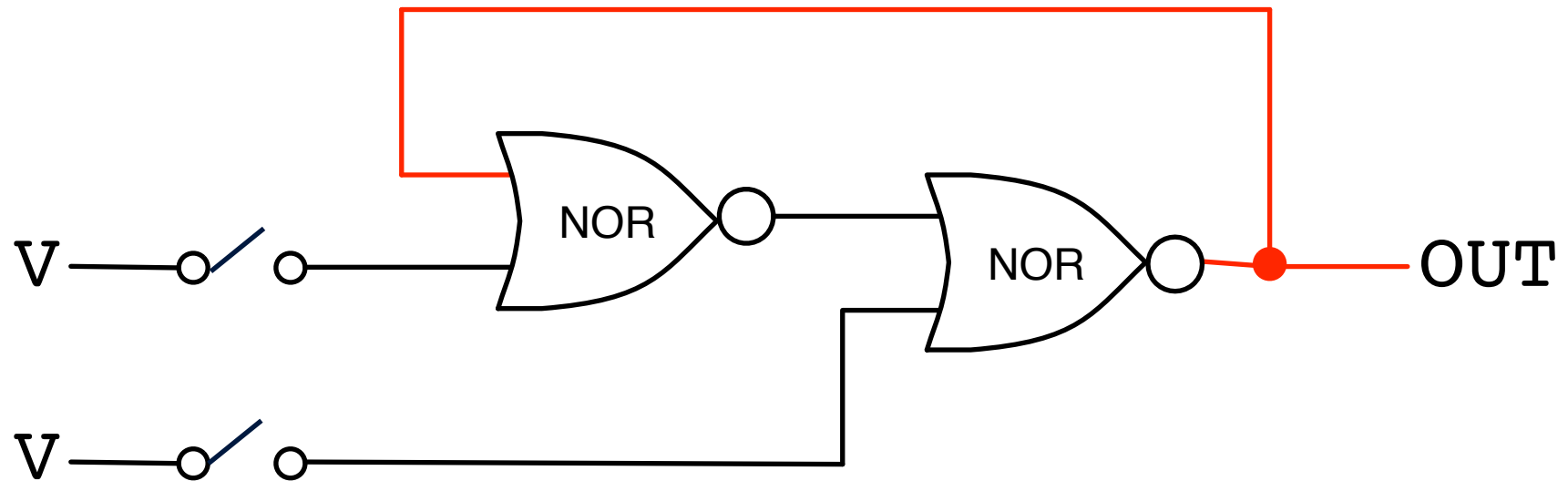


Same key configuration as initially

**But:** Now OUT is on --- we **remembered** the key turn


# Closing Lower Key

12

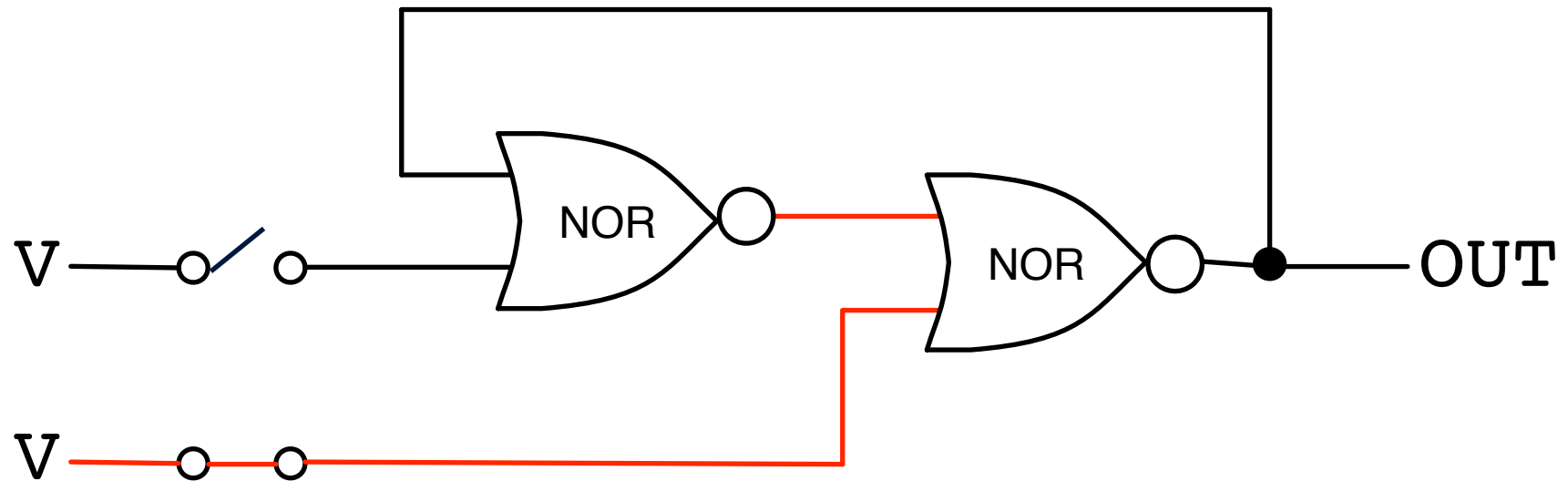

# Opening Lower Key

13

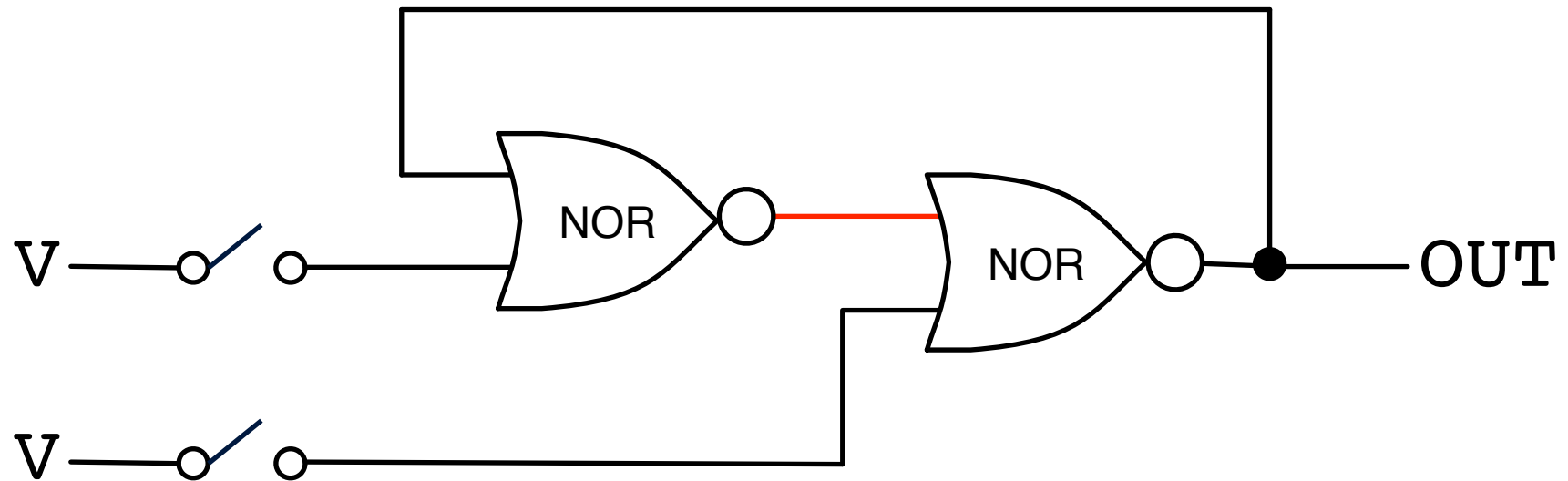

Back to initial state


- We have memory -- called **Reset-Set Flip-Flop**
- Truth table

UPPER	LOWER	OUT
0	0	OUT
0	1	0
1	0	1
1	1	Illegal

- UPPER = SET
- LOWER = RESET


# Re-Arranged

15

 

# Symmetric

16

 

# Truth Table

17



S	R	Q	$\bar{Q}$
1	0	1	0
0	1	0	1
0	0	Q	$\bar{Q}$
1	1	Illegal	






# d-type flip flop




- Control bit ("clock")
  - on = write to memory
  - off = read from memory
- Data bit
  - data item to be written
- Output
  - current state of the memory

# Replace Set/Reset with Data

 

# Add Control Bit ("Clock")

 

# D-Type Flip-Flop

- Also called **D-type latch**
- Circuit latches on one bit of memory and keeps it around
- Truth table

Data	Clock	Q	$\bar{Q}$
0	1	0	1
1	1	1	0
X	0	Q	$\bar{Q}$

- Can also build these for multiple data bits



# accumulative adder

# Design Goal


- Adder has initially value 0
- Adding a number  
→ value increases
- Resetting  
→ value goes back to 0

# Ingredients






# Ingredients

 

 
# Building an Accumulative Adder

- Latch: current sum
- Clock on  $\rightarrow$  set it to 0



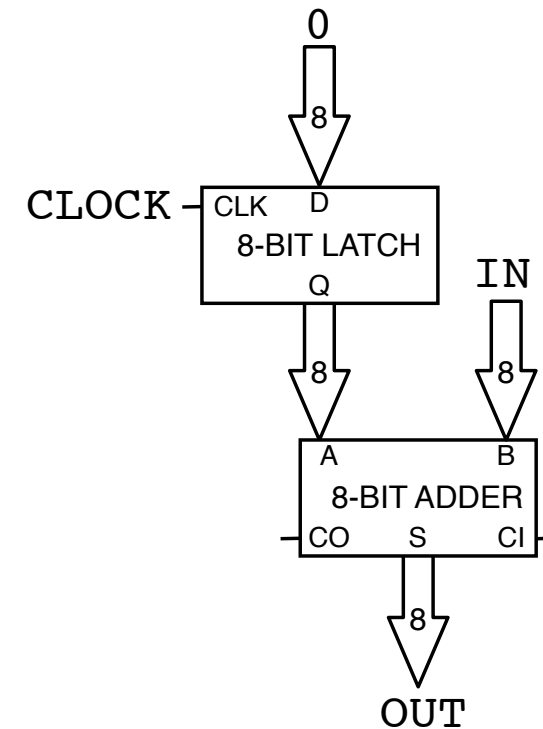
# Building an Accumulative Adder

- Adder
- Combines
  - current value
  - selected input



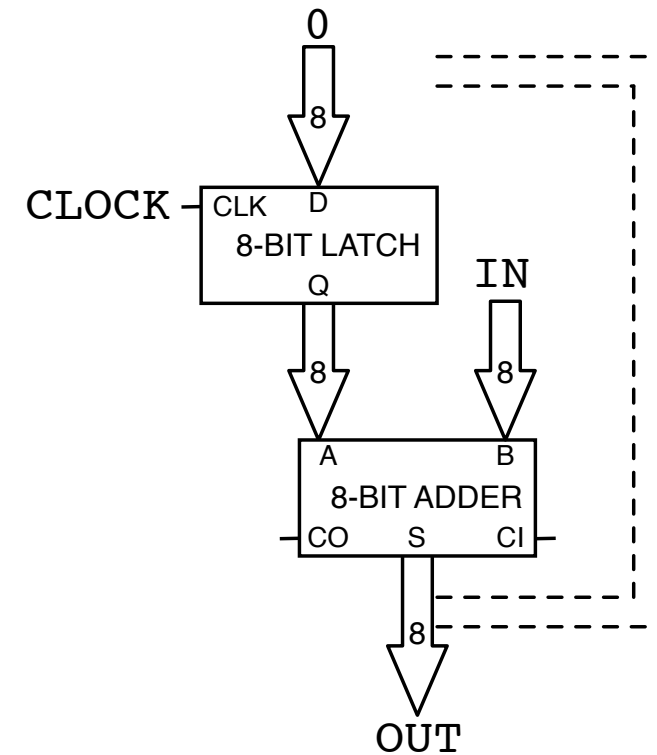
# Building an Accumulative Adder

- Can we pass output directly to latch?
- Concerns
  - select between 0 and sum
  - only stored when clock on



# Building an Accumulative Adder

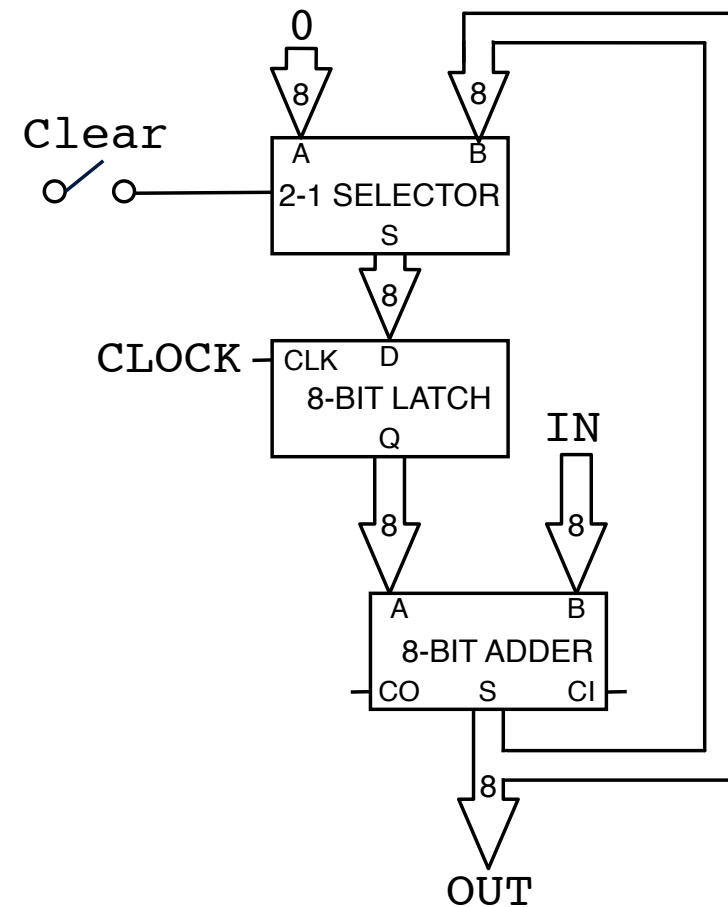- 2-1 selector
- Either uses 0 or sum
- Built with AND gates
- Still have runaway feedback loop...



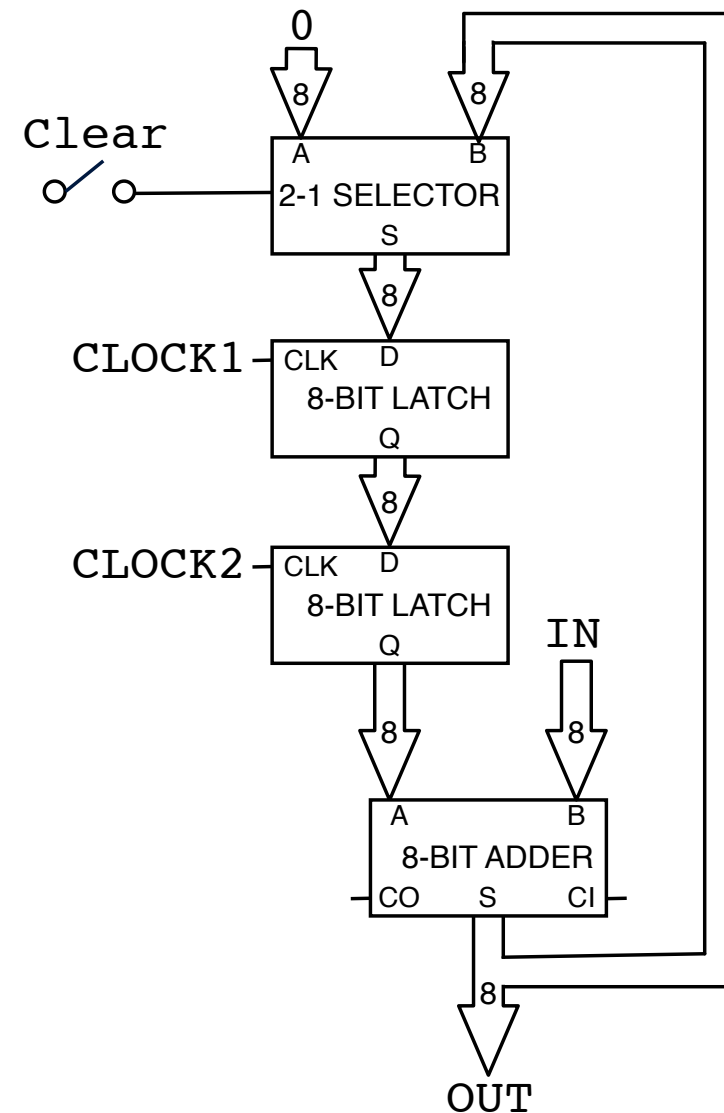
# Building an Accumulative Adder

31




- Two Latches
  - one to store the sum
  - one to store input to adder
- Clock 1
  - carry out addition
  - store result
- Clock 2
  - transfer to set up next addition


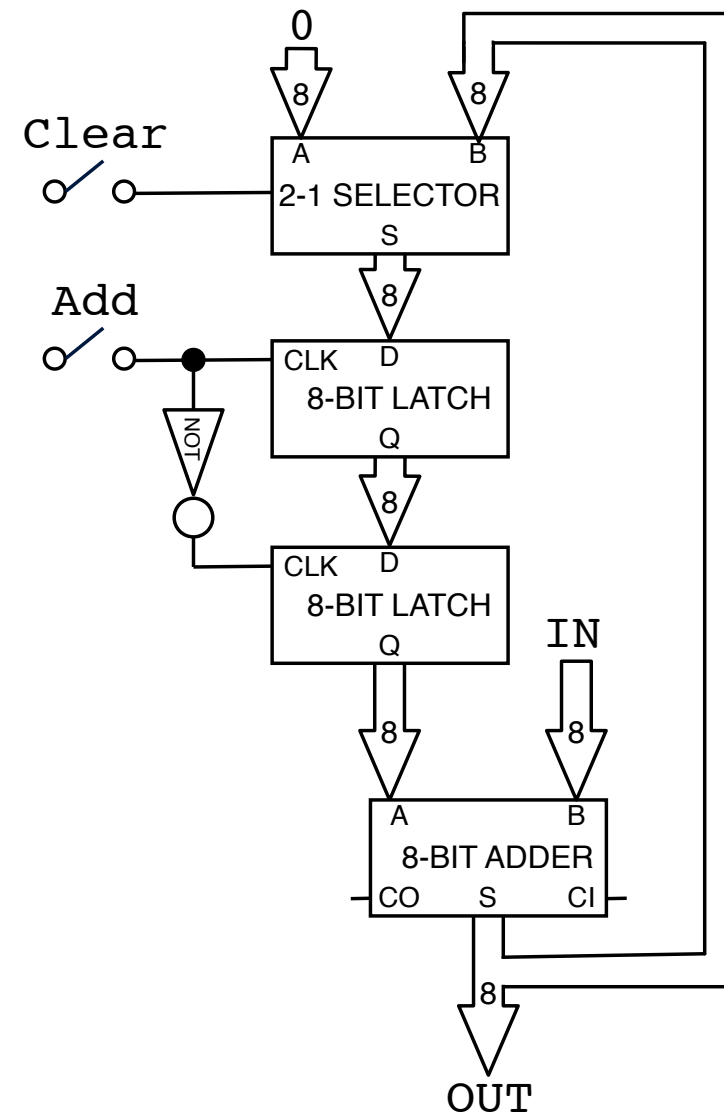
# Building an Accumulative Adder

- Combine the clocks
- Pressing the add key
  - carry out addition
  - store result in upper latch
- Release the add key
  - transfer to lower latch
  - set up next addition





# What Else?

33




- Remember the oscillator?

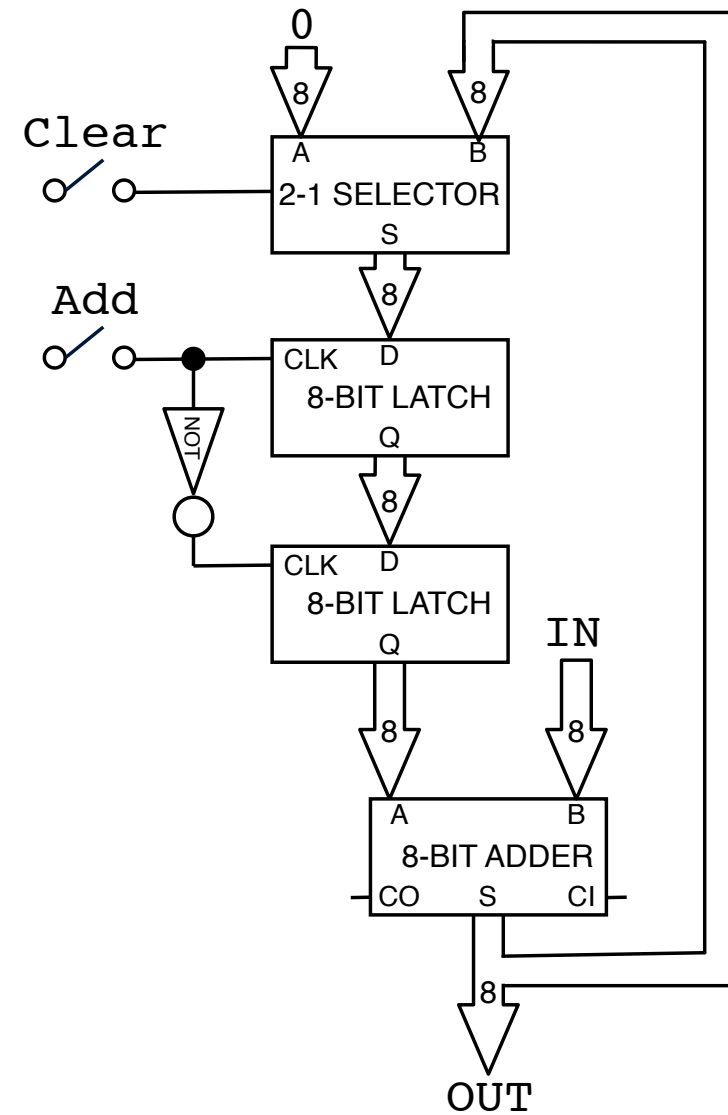 




# What Else?

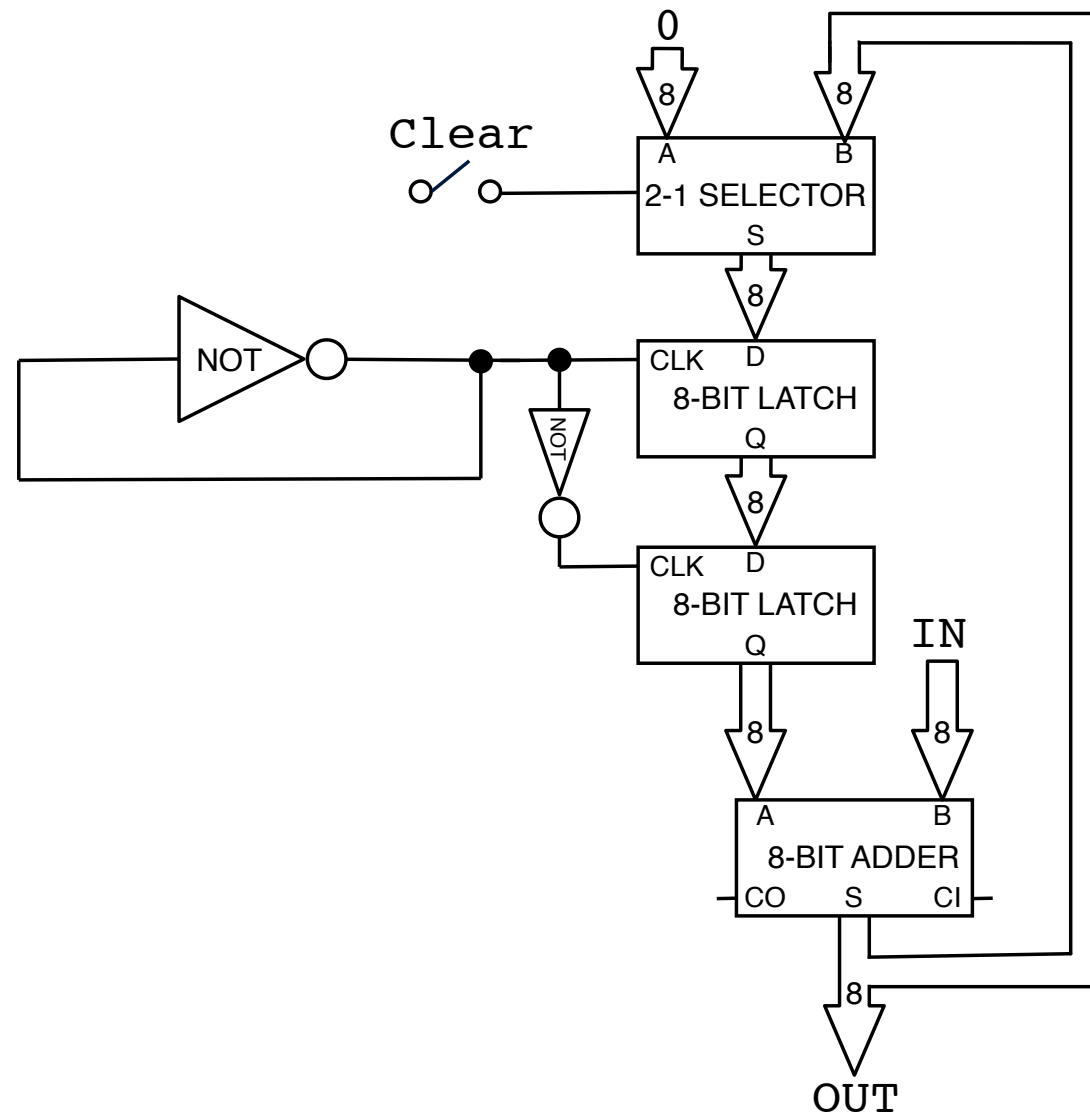

- Each cycle of oscillator:  
keeps adding

# What Else?

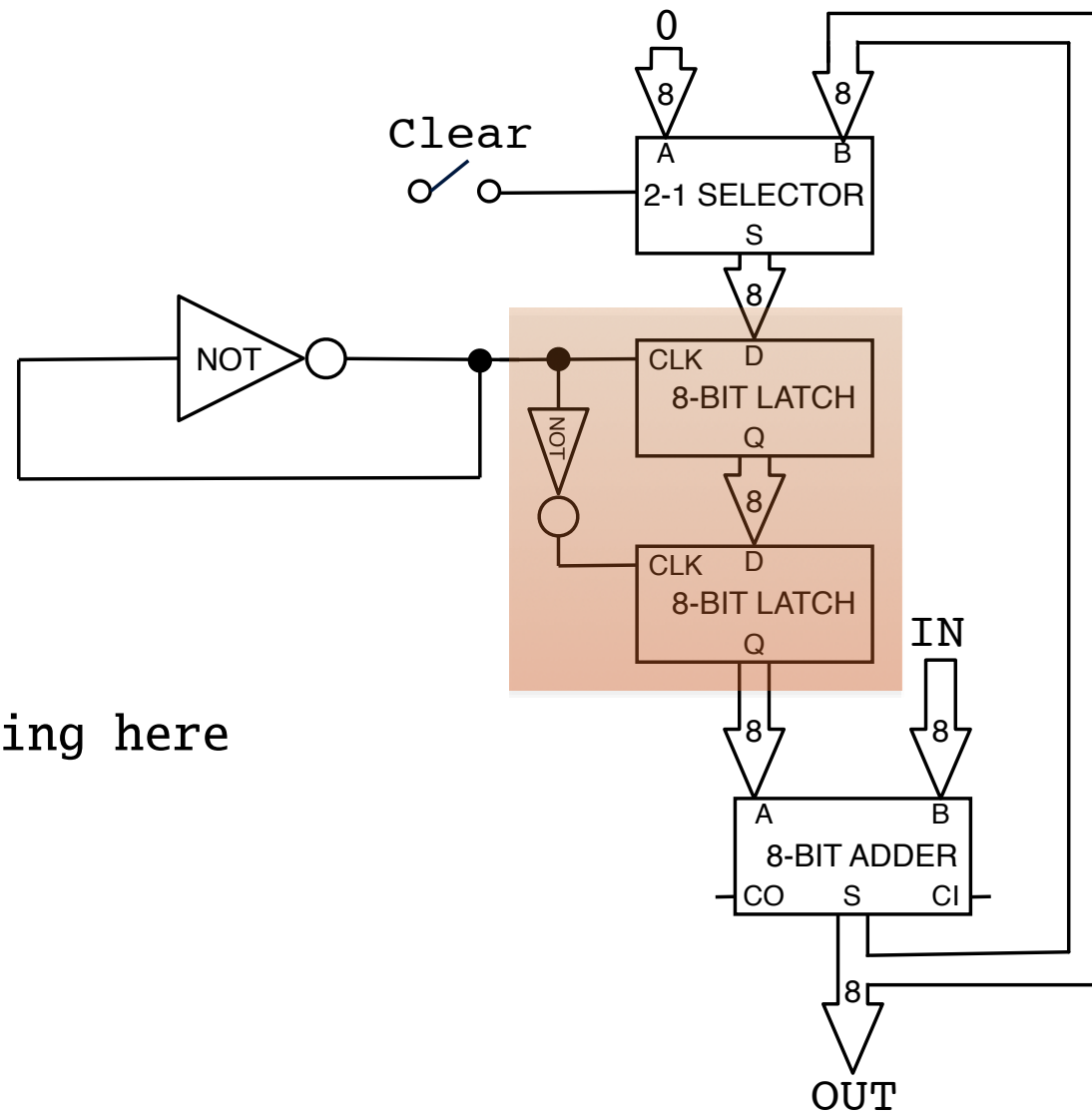

- We have something interesting here


# edge triggered flip-flop

# D-Type Latch




- When clock is on, save data
- "Level-triggered"

# D-Type Latch

 

- "Edge-triggered": changes value, when *switched from 0 to 1*

# Edge Triggered D-Type Latch

 

Symbol

# Truth Table


Data	Clock	Q	$\bar{Q}$
0	$\uparrow$	0	1
1	$\uparrow$	1	0
X	0	Q	$\bar{Q}$



# ripple counter




# Oscillator and Latch

 


Data	Clock	Q	$\bar{Q}$
1	0	0	1

# Oscillator and Latch

 


Data	Clock	Q	$\bar{Q}$
1	0	0	1
1	↑	1	0

# Oscillator and Latch

 

Data	Clock	Q	$\bar{Q}$
1	0	0	1
1	$\uparrow$	1	0
0	1	1	0


# Oscillator and Latch

 

Data	Clock	Q	$\bar{Q}$
1	0	0	1
1	$\uparrow$	1	0
0	1	1	0
0	0	1	0


# Oscillator and Latch

42

 


Data	Clock	Q	$\bar{Q}$
1	0	0	1
1	↑	1	0
0	1	1	0
0	0	1	0
0	↑	0	1

# Oscillator and Latch

 


Data	Clock	Q	$\bar{Q}$
1	0	0	1
1	↑	1	0
0	1	1	0
0	0	1	0
0	↑	0	1
1	1	0	1

# Oscillator and Latch

 

Data	Clock	Q	$\bar{Q}$
1	0	0	1
1	↑	1	0
0	1	1	0
0	0	1	0
0	↑	0	1
1	1	0	1
1	0	0	1


# Oscillator and Latch

 

Data	Clock	Q	$\bar{Q}$
1	0	0	1
1	↑	1	0
0	1	1	0
0	0	1	0
0	↑	0	1
1	1	0	1
1	0	0	1



# Oscillator and Latch

 


Data	Clock	Q	$\bar{Q}$
1	0	0	1
1	↑	1	0
0	1	1	0
0	0	1	0
0	↑	0	1
1	1	0	1
1	0	0	1


# Halving of Frequency

Data	Clock	Q	$\bar{Q}$
1	0	0	1
1	↑	1	0
0	1	1	0
0	0	1	0
0	↑	0	1
1	1	0	1
1	0	0	1



IN

 

OUT

 

# Multiple Bits

 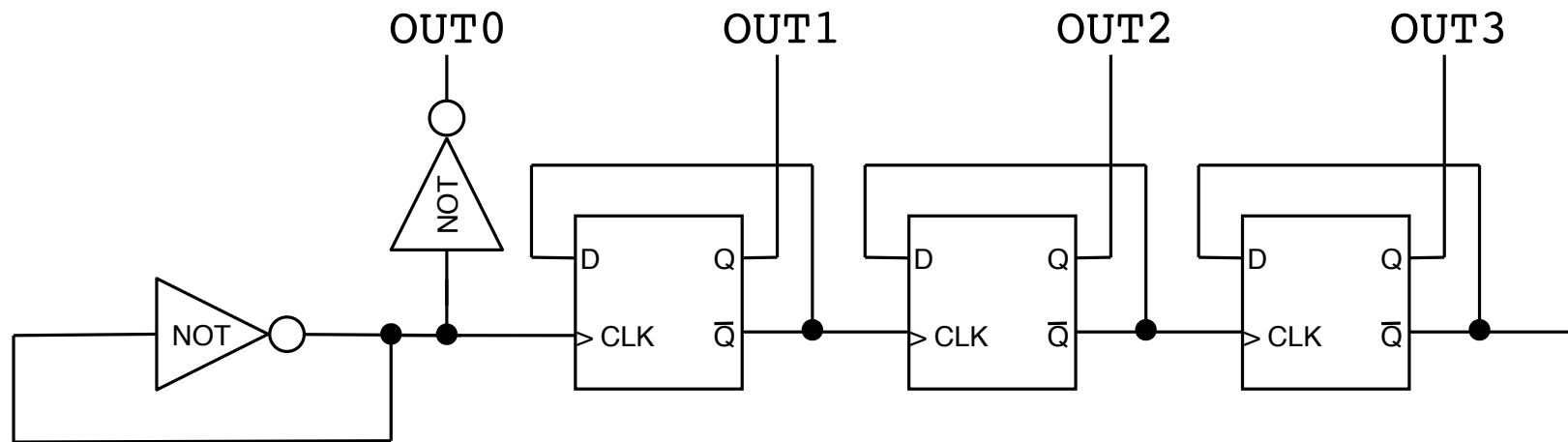

# Ripple Counter

46

