
Fast Arithmetic

Philipp Koehn
presented by Chang Hwan Choi

14 March 2018



arithmetic

Addition (Immediate)



- Load immediately one number ($s0 = 2$)

```
li $s0, 2
```

- Add 4 ($s1 = s0 + 4 = 6$)

```
addi $s1, $s0, 4
```

- Subtract 3 ($s2 = s1 - 3 = 3$)

```
addi $s2, $s1, -3
```

Addition (Register)



- Load immediately one number ($s0 = 2$)

```
li $s0, 2
```

- Add value from \$s5 ($s1 = s0 + s5$)

```
add $s1, $s0, $s5
```

- Subtract value from \$s6 ($s2 = s1 - s6$)

```
sub $s2, $s1, $s6
```

Overflow



- Signed integers operations: `add`, `addi`, and `sub`
 - overflow triggers exceptions
 - similar to interrupt
 - register `$mfc0` contains address of exception program
- Unsigned integers operations: `addu`, `addiu`, and `subu`
 - no overflow handling (as in C programming language)

Code for Detecting Overflow



5

- Overflow for unsigned integers operations can be detected from result
- Actual detection code is a bit intricate
- If you are interested
→ consult Section 3.2 in Patterson/Hennessy textbook

fast addition

Recall: N-Bit Addition


$$\begin{array}{r} 11 \\ +11 \\ \hline \hline \end{array}$$

Recall: N-Bit Addition



$$\begin{array}{r} 11 \\ +11 \\ \hline 1 \\ \hline 0 \end{array}$$

$1+1 = 0$, carry the 1

Recall: N-Bit Addition



$$\begin{array}{r} 11 \\ +11 \\ --- \\ 11 \\ --- \\ 10 \end{array}$$

$1+1+1 = 1$, carry the 1

Recall: N-Bit Addition

```
  11
+11
---
  11
---
 110
```

copy carry bit

Fast Addition

- We defined n-bit adding as a sequential process
- More bits \rightarrow addition takes longer
- 32 bit addition gets very slow
- Faster addition: Carry Lookahead

Problem: Carry Propagation

- 1+1 addition always causes a carry

$$1+1 + \text{carry}1 = 1, \text{ carry } 1$$

$$1+1 + \text{carry}0 = 0, \text{ carry } 1$$

- 0+0 addition never causes a carry

$$0+0 + \text{carry}1 = 1, \text{ carry } 0$$

$$0+0 + \text{carry}0 = 0, \text{ carry } 0$$

- 0+1 and 1+0 addition may cause a carry

$$0+1 + \text{carry}1 = 0, \text{ carry } 1$$

$$0+1 + \text{carry}0 = 1, \text{ carry } 0$$

Generate and Propagate

- Compute for each bit, if it generates or propagates carry
- Example

Operand A	0100	1111
Operand B	0110	0001
<hr/>		
Generate	0100	0001
Propagate	0110	1111
<hr/>		
Carry	1001	111-

- Generate: $a_i \text{ AND } b_i$
- Propagate: $a_i \text{ OR } b_i$
- Carry: ?



4-Bit Adder

14



- First compute generate and propagate for all bits
 - generate: $g_i = a_i \text{ AND } b_i$
 - propagate: $p_i = a_i \text{ OR } b_i$

4-Bit Adder

- First compute generate and propagate for all bits
 - generate: $g_i = a_i \text{ AND } b_i$
 - propagate: $p_i = a_i \text{ OR } b_i$
- Compute carries for each bit
 - $c_1 = g_0 \text{ OR } (p_0 \text{ AND } c_0)$

4-Bit Adder

- First compute generate and propagate for all bits
 - generate: $g_i = a_i \text{ AND } b_i$
 - propagate: $p_i = a_i \text{ OR } b_i$
- Compute carries for each bit
 - $c_1 = g_0 \text{ OR } (p_0 \text{ AND } c_0)$
 - $c_2 = g_1 \text{ OR } (p_1 \text{ AND } g_0) \text{ OR } (p_1 \text{ AND } p_0 \text{ AND } c_0)$

4-Bit Adder

- First compute generate and propagate for all bits
 - generate: $g_i = a_i \text{ AND } b_i$
 - propagate: $p_i = a_i \text{ OR } b_i$
- Compute carries for each bit
 - $c_1 = g_0 \text{ OR } (p_0 \text{ AND } c_0)$
 - $c_2 = g_1 \text{ OR } (p_1 \text{ AND } g_0) \text{ OR } (p_1 \text{ AND } p_0 \text{ AND } c_0)$
 - $c_3 = g_2 \text{ OR } (p_2 \text{ AND } g_1) \text{ OR } (p_2 \text{ AND } p_1 \text{ AND } g_1) \text{ OR } (p_2 \text{ AND } p_1 \text{ AND } p_0 \text{ AND } c_0)$
 - $c_4 = g_3 \text{ OR } (p_3 \text{ AND } g_2) \text{ OR } (p_3 \text{ AND } p_2 \text{ AND } g_2) \text{ OR } (p_3 \text{ AND } p_2 \text{ AND } p_1 \text{ AND } g_1) \text{ OR } (p_3 \text{ AND } p_2 \text{ AND } p_1 \text{ AND } p_0 \text{ AND } c_0)$
- The carry computations require no recursion
--- but use a lot of gates
- We may want to stop at 4 bits with this idea

16-Bit Adder

- Combine 4 4-bit adders
- For each 4-bit adder, compute
 - "super" propagate = $P = p_0 \text{ AND } p_1 \text{ AND } p_2 \text{ AND } p_3$

16-Bit Adder

- Combine 4 4-bit adders
- For each 4-bit adder, compute
 - "super" propagate = $P = p_0 \text{ AND } p_1 \text{ AND } p_2 \text{ AND } p_3$
 - "super" generate = $g_3 \text{ OR } (p_3 \text{ AND } g_2) \text{ OR } (p_3 \text{ AND } p_2 \text{ AND } g_1) \text{ OR } (p_3 \text{ AND } p_2 \text{ AND } p_1 \text{ AND } g_0)$

16-Bit Adder

- Combine 4 4-bit adders
- For each 4-bit adder, compute
 - "super" propagate = $P = p_0 \text{ AND } p_1 \text{ AND } p_2 \text{ AND } p_3$
 - "super" generate = $g_3 \text{ OR } (p_3 \text{ AND } g_2) \text{ OR } (p_3 \text{ AND } p_2 \text{ AND } g_1) \text{ OR } (p_3 \text{ AND } p_2 \text{ AND } p_1 \text{ AND } g_0)$
- Compute super carry C_j from super propagate P_j and super generate G_j
- Use C_j as input carry to the 4-bit adders

Cycles

1. compute propagate p_i and generate g_i
2. compute carry c_i
compute super propagate P_j and super generate G_j
3. compute super carry C_j
4. carry out all bitwise additions

- Higher n in n -bit adders
 - more gates in circuit
 - faster computation
- Modern CPUs can pack more gates on a chip
 - \Rightarrow speed-up at same clock speed



multiplication

Recall Method

19



- Elementary school multiplication:

$$10101 \times 1101$$

Recall Method

- Elementary school multiplication:

$$\begin{array}{r} 10101 \times 1101 \\ \hline 10101 \end{array}$$

Recall Method

- Elementary school multiplication:

$$\begin{array}{r} 10101 \times 1101 \\ \hline 10101 \\ 0 \\ \hline \end{array}$$

Recall Method

- Elementary school multiplication:

$$\begin{array}{r} 10101 \times 1101 \\ \hline 10101 \\ 0 \\ 10101 \\ \hline \end{array}$$

Recall Method

- Elementary school multiplication:

$$\begin{array}{r} 10101 \times 1101 \\ \hline 10101 \\ 0 \\ 10101 \\ 10101 \end{array}$$

Recall Method

- Elementary school multiplication:

$$\begin{array}{r} 10101 \times 1101 \\ \hline 10101 \\ 0 \\ 10101 \\ 10101 \\ \hline 100010001 \end{array}$$

(in decimal: $23 \times 13 = 299$)

Recall Method


- Elementary school multiplication:

$$\begin{array}{r} 10101 \times 1101 \\ \hline 10101 \\ 0 \\ 10101 \\ 10101 \\ \hline 100010001 \end{array}$$

(in decimal: $23 \times 13 = 299$)

- Idea
 - shift second operand to right (get last bit)
 - if carry: add second operand to sum
 - rotate first operand to left (multiply with binary 10)

Multiplication in Hardware

 


- Control unit runs microprogram

loop 32 times:

- if lowest bit of multiplier=1
 - add multiplicand to product
 - shift multiplicand left
 - shift multiplier right

- Note: multiplying 32 bit numbers may result in 64 bit product

Multiplication in Hardware

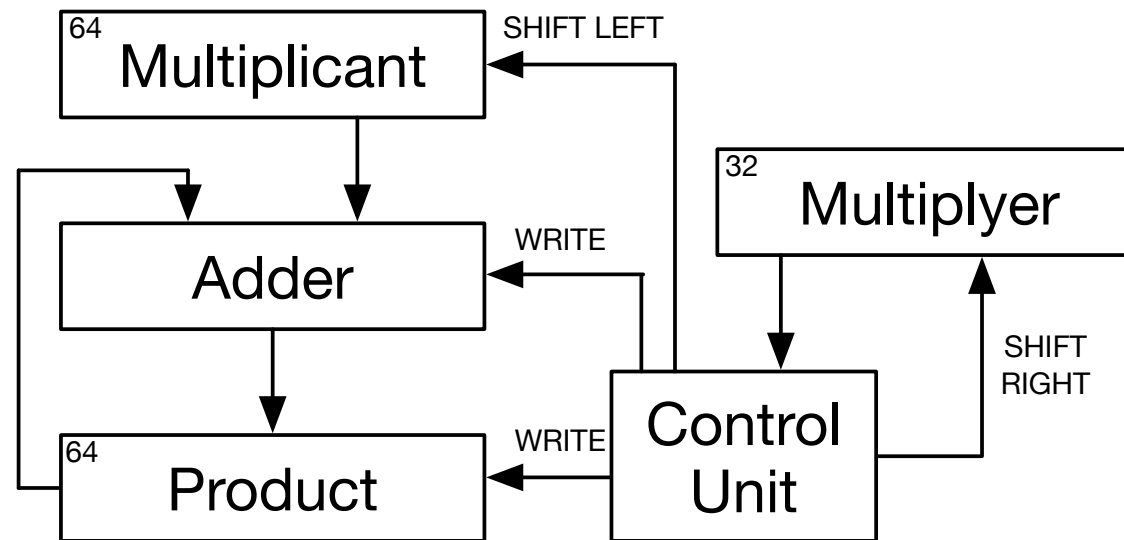

- Control unit runs microprogram

loop 32 times:

- if lowest bit of multiplier=1
 - add multiplicand to product
 - shift multiplicand left
 - shift multiplier right

- Speed

- 32 iterations
 - 3 operations each
(add + shift + shift)
- almost 100 operations

- Note: multiplying 32 bit numbers may result in 64 bit product

Parallelize the 3 Operations

- The 3 operations in each loop affect different registers
 - add: product
 - shift left: multiplicand
 - shift right: multiplier

⇒ These can be executed in parallel
(note: read is executed before write)

Parallelize the Iterations



22


- Sum of 32 independently computed values

Parallelize the Iterations

- Sum of 32 independently computed values
- More adders \rightarrow some summing can be done in parallel

Parallelize the Iterations

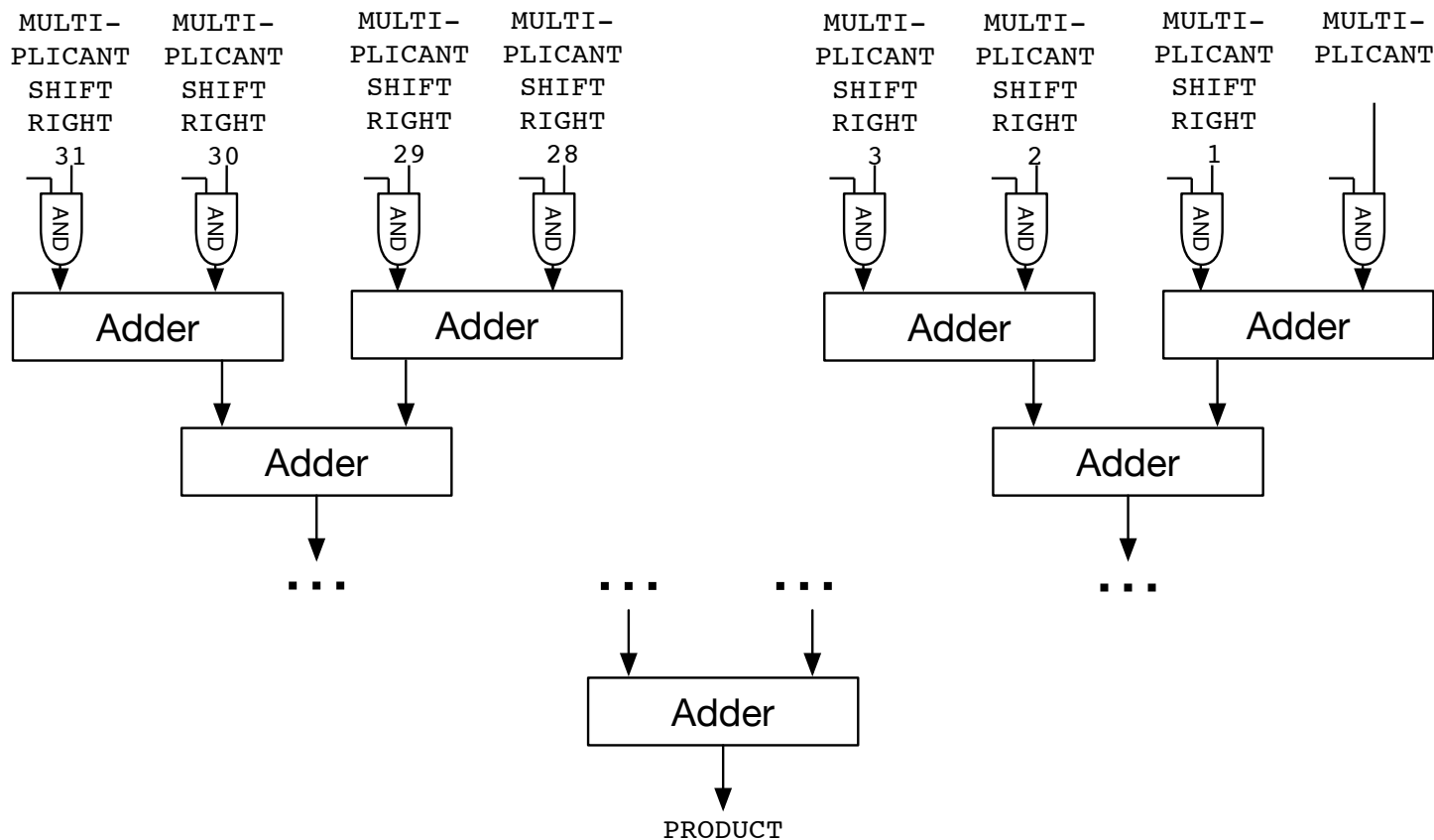- Sum of 32 independently computed values
- More adders \rightarrow some summing can be done in parallel
- Binary tree $\rightarrow \log_2 32 = 5$ cycles



MIPS Instructions

- 32 bit multiplication results in 64 bit product

MIPS Instructions

- 32 bit multiplication results in 64 bit product
- Special 64 bit register holds result
 - hi: high word
 - lo: low word

MIPS Instructions

- 32 bit multiplication results in 64 bit product
- Special 64 bit register holds result
 - hi: high word
 - lo: low word
- Low word has to be retrieved by another instruction

```
mult $s1, $s2  
mflo $s0
```


MIPS Instructions

- 32 bit multiplication results in 64 bit product
- Special 64 bit register holds result
 - hi: high word
 - lo: low word
- Low word has to be retrieved by another instruction

```
mult $s1, $s2  
mflo $s0
```

- Since this is the typical usage, pseudo-instruction

```
mul $s0, $s1, $s2
```

More on that later

division

Elementary School Division



$$1011 \div 10 =$$

Elementary School Division

25



$$\begin{array}{r} 1011 \text{ / } 10 = \\ 10 \end{array}$$

Elementary School Division

25



$$\begin{array}{r} 1011 \div 10 = 1 \\ 10 \\ \hline 0 \end{array}$$

Elementary School Division

25



$$\begin{array}{r} 1011 \div 10 = 10 \\ 10 \\ \hline 0 \\ 01 \end{array}$$

Elementary School Division

25



$$\begin{array}{r} 1011 \div 10 = 10 \\ 10 \\ \hline 0 \\ 01 \\ 011 \end{array}$$

Elementary School Division

25



$$\begin{array}{r} 1011 \div 10 = 101 \\ 10 \\ \hline 0 \\ 01 \\ 011 \\ 10 \\ \hline 1 \text{ Remainder} \end{array}$$

$$\begin{array}{r} 1011 \text{ / } 10 = 101 \\ \underline{10} \\ 0 \\ 01 \\ \underline{011} \\ 10 \\ \underline{} \\ 1 \text{ Remainder} \end{array}$$

- Algorithm

1. shift divisor sufficiently to the left
2. check if subtraction is possible
 - yes \rightarrow add result bit 1, carry out subtraction
 - no \rightarrow add result bit 0
3. pull down bit from dividend
4. shift divisor to the right
 - not possible \rightarrow done, note remainder
 - otherwise go to step 2

Algorithm Refinement

1. Shift divisor sufficiently to the left

- hard for machine to determine
- shift to maximum left
- 32 bit division: use 64 register, push 32 positions

Algorithm Refinement

1. Shift divisor sufficiently to the left
 - hard for machine to determine
 - shift to maximum left
 - 32 bit division: use 64 register, push 32 positions
2. Check if subtraction is possible
 - yes → add result bit 1, carry out subtraction
 - no → add result bit 0
 - we always carry out subtraction
 - if overflow, do not use result

Algorithm Refinement

1. Shift divisor sufficiently to the left
 - hard for machine to determine
 - shift to maximum left
 - 32 bit division: use 64 register, push 32 positions
2. Check if subtraction is possible
 - yes → add result bit 1, carry out subtraction
 - no → add result bit 0
 - we always carry out subtraction
 - if overflow, do not use result
3. Pull down bit from dividend

Algorithm Refinement

1. Shift divisor sufficiently to the left
 - hard for machine to determine
 - shift to maximum left
 - 32 bit division: use 64 register, push 32 positions
2. Check if subtraction is possible
 - yes → add result bit 1, carry out subtraction
 - no → add result bit 0
 - we always carry out subtraction
 - if overflow, do not use result
3. Pull down bit from dividend
4. Shift divisor to the right
 - not possible → done, note remainder
 - otherwise go to step 2

Division in Hardware

- Operations similar to multiplication
 - shift divisor
 - subtraction
 - indication if subtraction should be accepted
- These operations can be parallelized
- But: iterations cannot be parallelized the same way
(sophisticated prediction methods guess outcome of subtractions)

MIPS Instructions



- 32 bit division results in 32 bit quotient and 32 bit remainder
 - hi: remainder
 - lo: quotient

MIPS Instructions

- 32 bit division results in 32 bit quotient and 32 bit remainder
 - hi: remainder
 - lo: quotient
- Quotient has to be retrieved by another instruction

```
div $s1, $s2  
mflo $s0
```


- 32 bit division results in 32 bit quotient and 32 bit remainder
 - hi: remainder
 - lo: quotient
- Quotient has to be retrieved by another instruction

```
div $s1, $s2  
mflo $s0
```