 

Memory

Philipp Koehn


9 September 2019



D-Type Level-Triggered Latch



Slightly Modified

 

Operations




- Circuit latches on one bit of memory and keeps it around
- Truth table

Data-In	Write	Data-Out
0	1	0
1	1	1
X	0	Data


- Can write 1 bit and read content

multi-bit storage

1 Bit Memory

 

8 Bit Memory

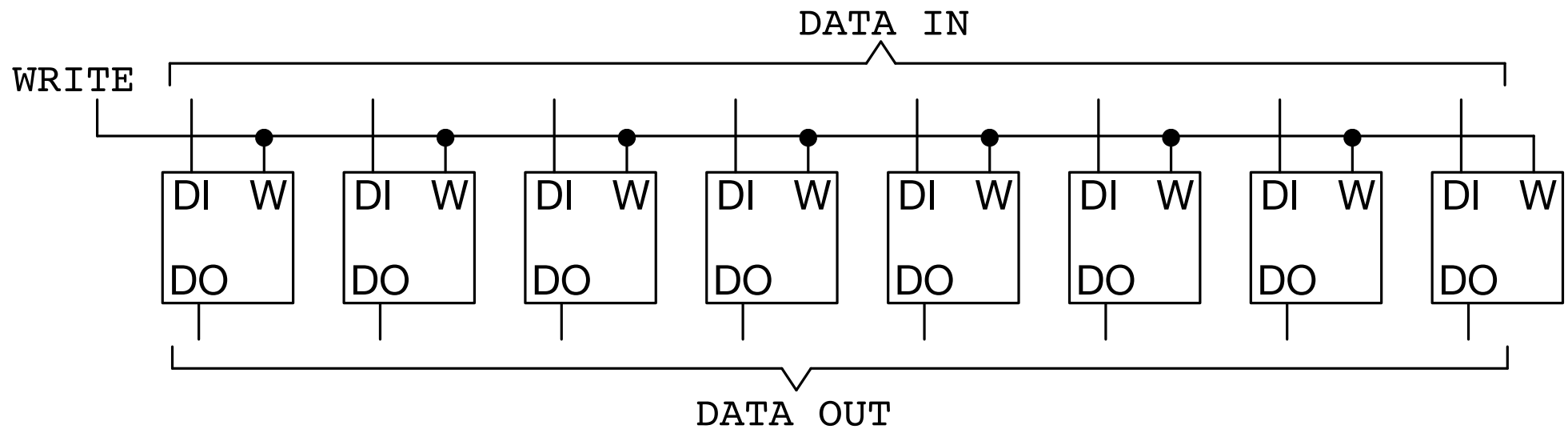


Output Selector



- 8 Bit Latch contains 8 bits
- Now: only read 1 bit at a time
- Select the bit with an address
- Input: address
- Output: bit value

Output Selector

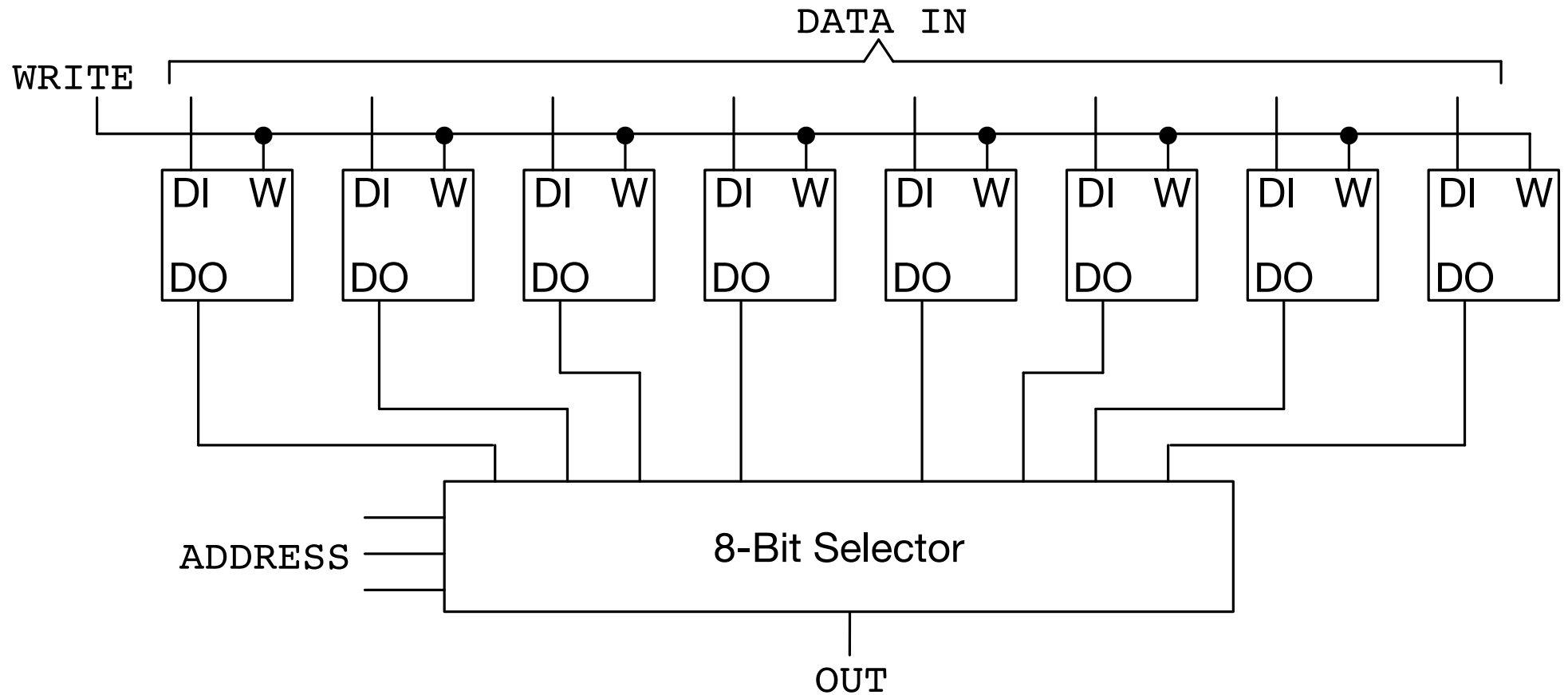

Output Selector

- Truth table

Address			Output
A2	A1	A0	OUT
0	0	0	D ₀
0	0	1	D ₁
0	1	0	D ₂
0	1	1	D ₃
1	0	0	D ₄
1	0	1	D ₅
1	1	0	D ₆
1	1	1	D ₇

Output Selector

- Truth table

Address			Output
A2	A1	A0	OUT
0	0	0	D ₀
0	0	1	D ₁
0	1	0	D ₂
0	1	1	D ₃
1	0	0	D ₄
1	0	1	D ₅
1	1	0	D ₆
1	1	1	D ₇

- What Boolean operation returns the correct value for address 000?

Output Selector

- Truth table

Address			Output
A2	A1	A0	OUT
0	0	0	D ₀
0	0	1	D ₁
0	1	0	D ₂
0	1	1	D ₃
1	0	0	D ₄
1	0	1	D ₅
1	1	0	D ₆
1	1	1	D ₇

- What Boolean operation returns the correct value for address 000?
(NOT A2) AND (NOT A1) AND (NOT A0) AND D0


Output Selector

- Full Boolean formula

```
( (NOT A2) AND (NOT A1) AND (NOT A0) AND D0 ) OR
( (NOT A2) AND (NOT A1) AND      A0  AND D1 ) OR
( (NOT A2) AND      A1  AND (NOT A0) AND D2 ) OR
( (NOT A2) AND      A1  AND      A0  AND D3 ) OR
(      A2  AND (NOT A1) AND (NOT A0) AND D4 ) OR
(      A2  AND (NOT A1) AND      A0  AND D5 ) OR
(      A2  AND      A1  AND (NOT A0) AND D6 ) OR
(      A2  AND      A1  AND      A0  AND D7 )
```

Output Selector


11

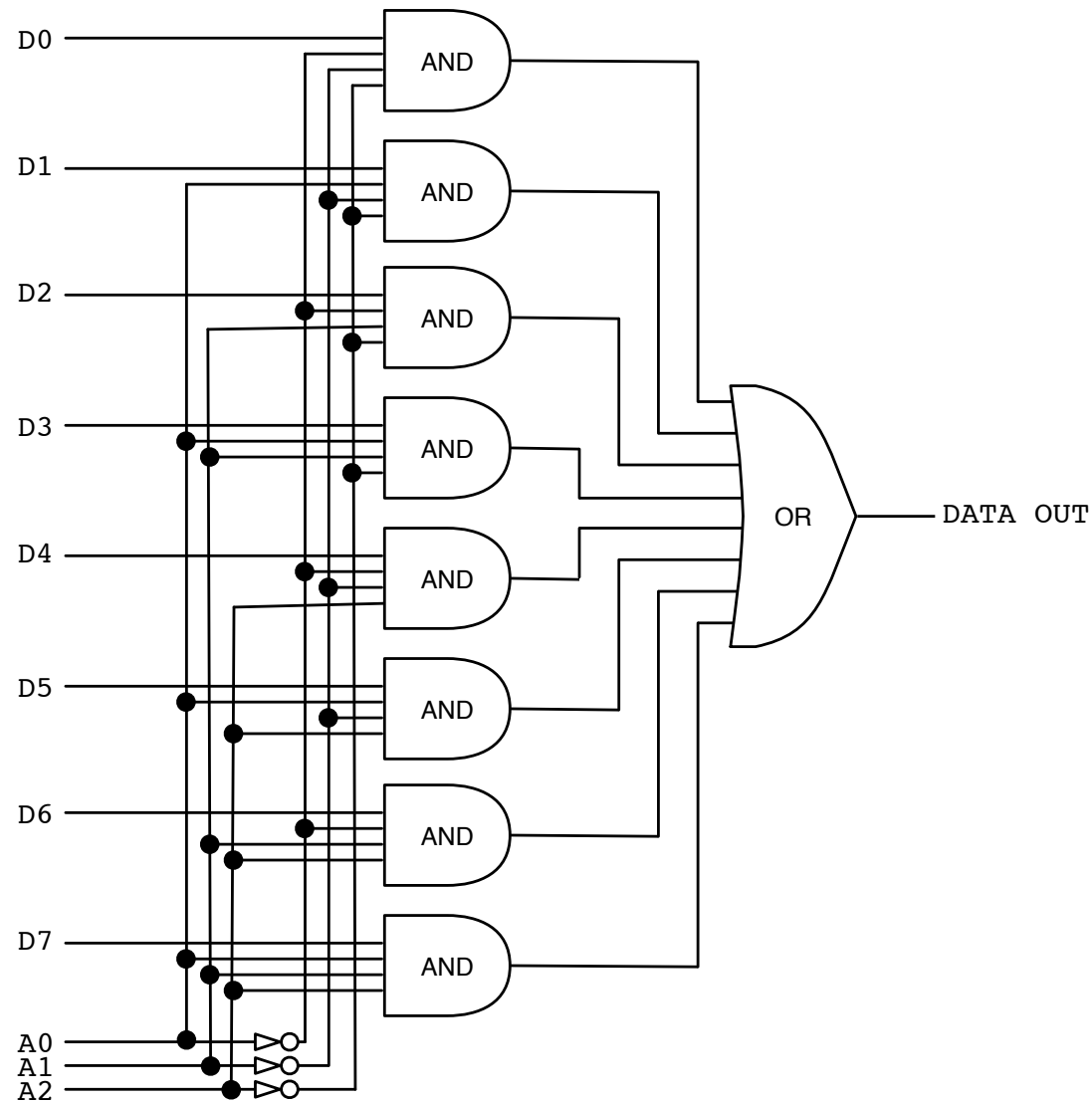

Input Decoder

- 8 Bit Latch allows 8 bits to be written at the same time
- Now: only write 1 bit at a time
- Select the bit with an address
- Input
 - address
 - write flag
 - data bit

Input Decoder

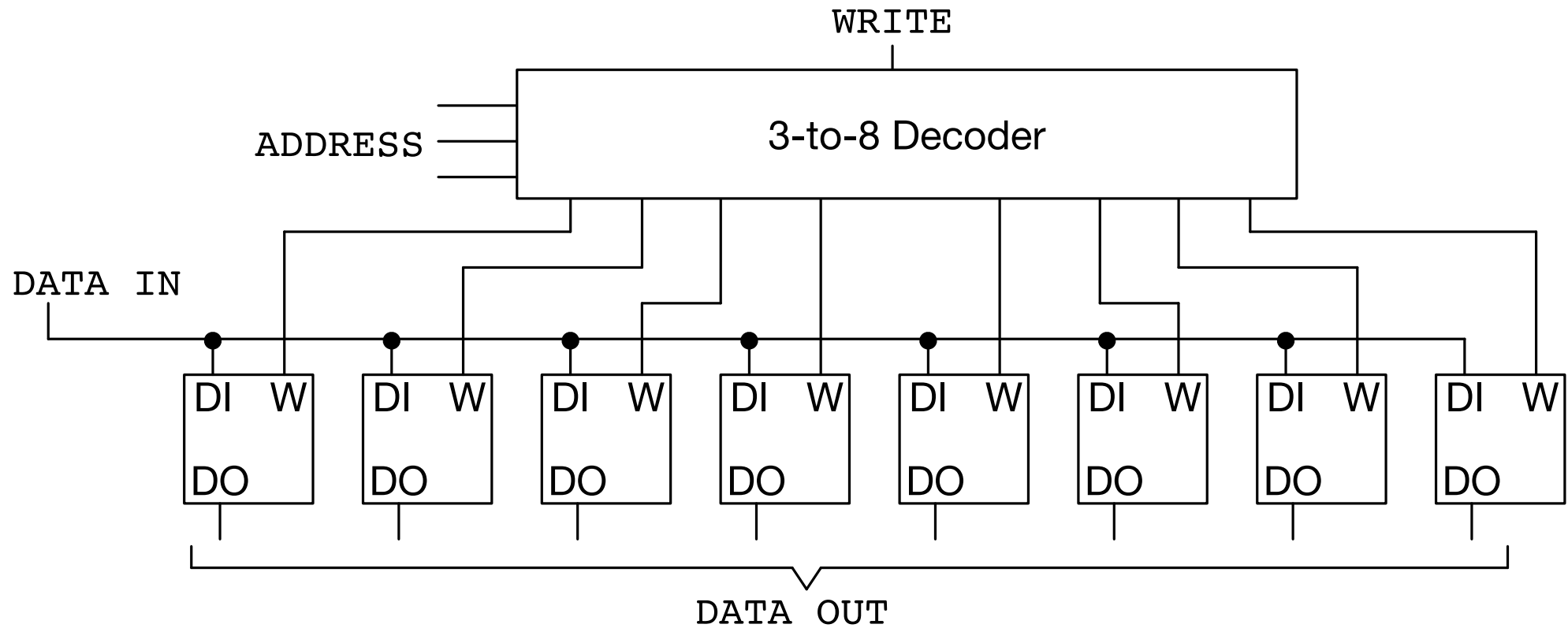

Input Decoder

- Truth table

Address			Output							
A2	A1	A0	W7	W6	W5	W4	W3	W2	W1	W0
0	0	0	0	0	0	0	0	0	0	WRITE
0	0	1	0	0	0	0	0	0	WRITE	0
0	1	0	0	0	0	0	0	WRITE	0	0
0	1	1	0	0	0	0	WRITE	0	0	0
1	0	0	0	0	0	WRITE	0	0	0	0
1	0	1	0	0	WRITE	0	0	0	0	0
1	1	0	0	WRITE	0	0	0	0	0	0
1	1	1	WRITE	0	0	0	0	0	0	0

- What Boolean operation returns the correct value for output W0?

Input Decoder


- Truth table

Address			Output							
A2	A1	A0	W7	W6	W5	W4	W3	W2	W1	W0
0	0	0	0	0	0	0	0	0	0	WRITE
0	0	1	0	0	0	0	0	0	WRITE	0
0	1	0	0	0	0	0	0	WRITE	0	0
0	1	1	0	0	0	0	WRITE	0	0	0
1	0	0	0	0	0	WRITE	0	0	0	0
1	0	1	0	0	WRITE	0	0	0	0	0
1	1	0	0	WRITE	0	0	0	0	0	0
1	1	1	WRITE	0	0	0	0	0	0	0


- What Boolean operation returns the correct value for output W0?

(NOT A2) AND (NOT A1) AND (NOT A0) AND WRITE

Input Decoder

 

8 Bit RAM

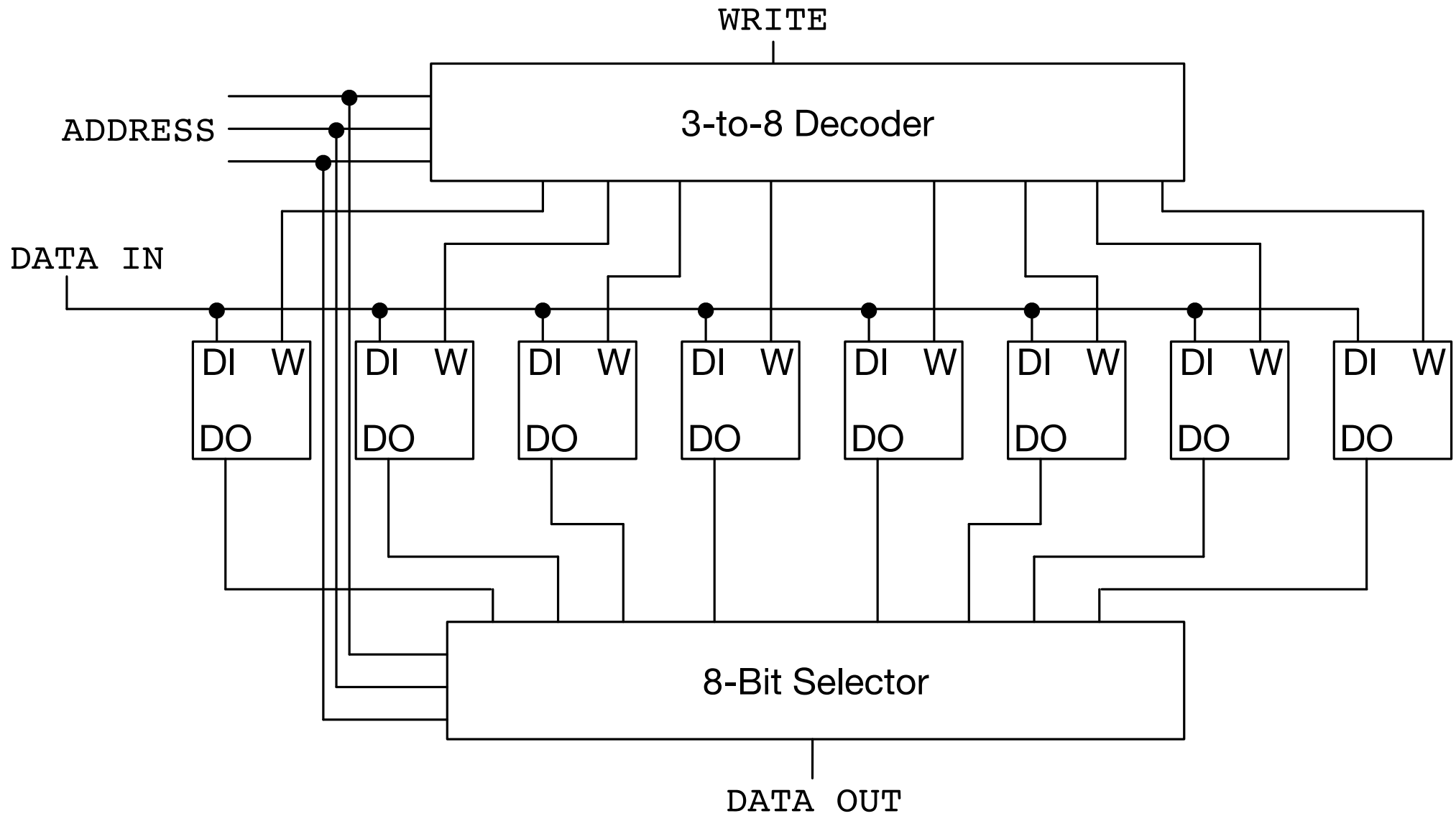

8 Bit RAM


- 8 Bit Random Access Memory (RAM)

- Input

- address
- write flag
- data bit

- Output

- data bit

 

8x2 Bit RAM


- 8x1 bit RAM allows read/write of 1 bit at a time
- What if we want to read/write 2 bits at a time?
(and ultimately 8 bits (1 byte) and more)

8x2 Bit RAM


- 8x1 bit RAM allows read/write of 1 bit at a time
- What if we want to read/write 2 bits at a time?
(and ultimately 8 bits (1 byte) and more)

⇒ Arrange them together


8x2 Bit RAM

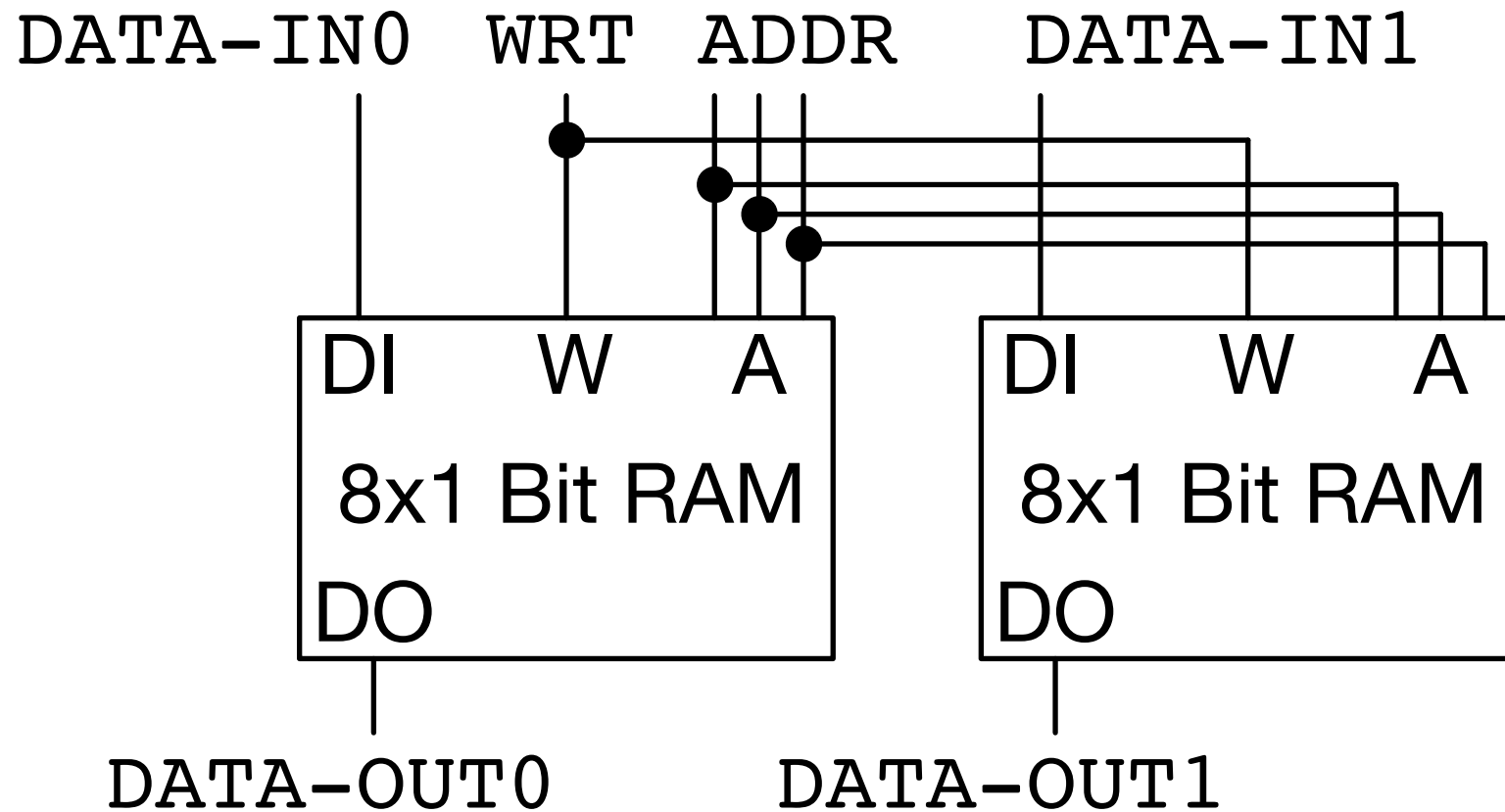


8x2 Bit RAM

 

8x2 Bit RAM

 


64 KB RAM

 

- 64KB = 65,536 bytes
- 16 bit address space ($2^{16} = 65536$)
- Common memory size in the 1980s: we will use it with 6502 assembly

Control Panel

23

 

Memories

```
**** COMMODORE 64 BASIC V2 ****  
64K RAM SYSTEM 38911 BASIC BYTES FREE  
READY.
```

Early 1980s: 64 KB RAM, 16 bit address space

Bigger Memories

- Early 1980s: 16 bit address space, up to 64 KB

Bigger Memories

- Early 1980s: 16 bit address space, up to 64 KB
- 1990s: 32-bit address space, up to 4 GB

Bigger Memories

- Early 1980s: 16 bit address space, up to 64 KB
- 1990s: 32-bit address space, up to 4 GB
- Today: 64-bit address space, up to 16 EB (exa-byte)

Bigger Memories

- Early 1980s: 16 bit address space, up to 64 KB
- 1990s: 32-bit address space, up to 4 GB
- Today: 64-bit address space, up to 16 EB (exa-byte)
- Actually supported by Intel/AMD 64-bit processors
 - 52 bits for physical memory: 4 peta-byte
 - 48 bits for virtual memory: 256 tera-byte

Bigger Memories

- Early 1980s: 16 bit address space, up to 64 KB
- 1990s: 32-bit address space, up to 4 GB
- Today: 64-bit address space, up to 16 EB (exa-byte)
- Actually supported by Intel/AMD 64-bit processors
 - 52 bits for physical memory: 4 peta-byte
 - 48 bits for virtual memory: 256 tera-byte
- Actually existing RAM: my lab biggest RAM machine: 768 GB (doubles every ~ 2 years)